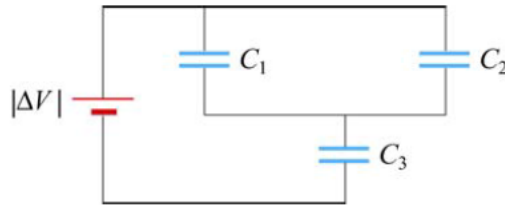


## Question bank three

### Capacitors and dielectrics

#### Question 1.

Find the equivalent capacitance for the combination of capacitors shown in Figure below




Capacitor connected in series and parallel (mixed)

#### Solution:

Since  $C_1$  and  $C_2$  are connected in parallel, their equivalent capacitance

$C_{12}$  is given by

$$C_{12} = C_1 + C_2$$

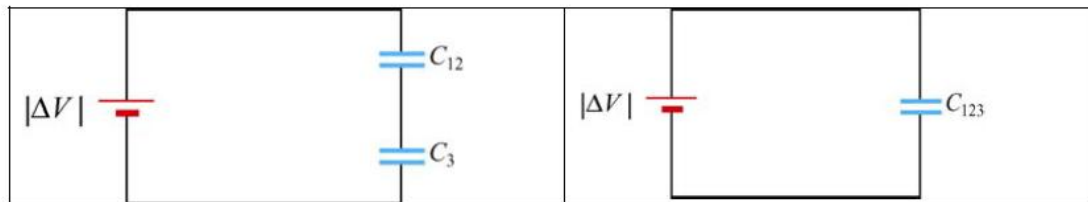

Now capacitor  $C_{12}$  is in series with  $C_3$ , So, the equivalent capacitance

$C_{123}$  is given by

$$\frac{1}{C_{123}} = \frac{1}{C_1} + \frac{1}{C_2}$$
$$C_{123} = \frac{C_{12} C_3}{C_{12} + C_3} = \frac{(C_1 + C_2)C_3}{C_1 + C_2 + C_3}$$

**Question 2** a parallel plate capacitor of capacitance  $4\mu\text{F}$  carries a charge of  $600\mu\text{C}$ . What is the potential difference between the plates of the capacitor?

Solution:

$$\Delta V = \frac{Q}{C} \quad \text{THUS}$$

$$\Delta V = \frac{600\mu\text{C}}{4\mu\text{F}} = \mathbf{15\text{ V}}$$

**Question 3** a parallel plate capacitor has an area of  $40\text{ cm} \times 50\text{ cm}$  and plates separated by  $1\text{ cm}$ .

- What is the capacitance of this capacitor in unit of farad?
- If it has a charge of  $3.6 \times 10^{-3}\text{ C}$ , what is the potential difference across the capacitor?

Solution:

$$\text{a.} \quad C = \frac{\epsilon_0 A}{d}$$

$$C = \frac{\left(8.85 \times 10^{-12} \frac{\text{F}}{\text{m}}\right) ((0.4\text{m})(0.5\text{m}))}{0.01\text{m}} = \mathbf{18 \times 10^{-11}\text{ F}}$$

$$= \mathbf{180\text{ pF}}$$

$$\text{b.} \quad \Delta V = \frac{Q}{C} = \frac{3.6 \times 10^{-3}\text{ C}}{18 \times 10^{-11}\text{ F}} = \mathbf{2 \times 10^7\text{ Volts}}$$


**Question 4** two capacitors  $C_1$  and  $C_2$  are connected in series, find:

- The equivalent capacitance
- the total charge
- the charge on each capacitor
- the voltage across each capacitor.

Solution:

$$\text{a.} \quad \frac{1}{C_{eq}} = \frac{1}{C_1} + \frac{1}{C_2}$$
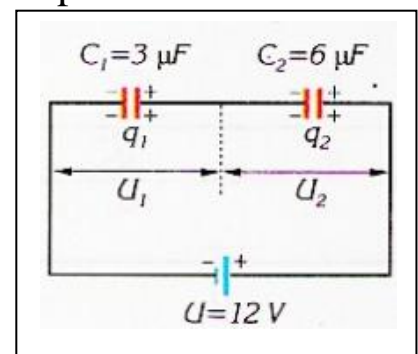
$$\frac{1}{C_{eq}} = \frac{1}{3} + \frac{1}{6} = \frac{3}{6}, \quad C_{eq} = \mathbf{2\mu\text{F}}$$



**b.**  $Q_t = C_{eq} \Delta V = (2\mu F)(12V) = 24\mu C$

**c.** Since the charge on each capacitor in a series circuit is equal to the total charge,

$$Q_t = Q_1 = Q_2$$

**d.**  $Q_1 = C_1 \Delta V_1, 24\mu C = 2\mu F \Delta V_1 \rightarrow \Delta V_1 = 8V$

$Q_2 = C_2 \Delta V_2, 24\mu C = 6\mu F \Delta V_2 \rightarrow \Delta V_2 = 4V$

**Question 5** two capacitors  $C_1 = 1\mu F$  and  $C_2 = 2\mu F$  are connected in parallel, find:

- a. The equivalent capacitance    b. the total charge    c. potential difference across each capacitor and    d. the charge on each capacitor.


Solution:

**a.**  $C_{eq} = C_1 + C_2$

$C_{eq} = 1 + 2 = 3\mu F$

**b.**  $Q_t = C_{eq} \Delta V$

$Q_t = (3\mu F)(12V) = 36\mu C$

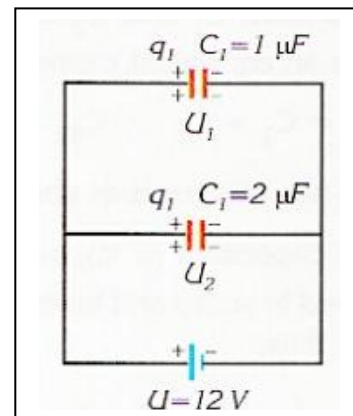

**c.** In parallel connection the potential difference across each capacitor is equal to the total potential difference of the circuit.

So,

$$\Delta V_t = \Delta V_1 = \Delta V_2 = 12V$$

**d.**  $Q = C \Delta V$

$Q_1 = C_1 \Delta V_1 = 1 * 12 = 12\mu C$   
 $12 = 24\mu C$


$Q_2 = C_2 \Delta V_2 = 2 * 12 = 24\mu C$

$Q_t = Q_1 + Q_2 = 12 + 24 = 36 \mu C$
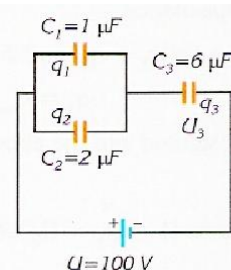
## Question 6

Three capacitors of capacitance  $C_1=1\ \mu\text{F}$ ,  $C_2=2\ \mu\text{F}$  and  $C_3=6\ \mu\text{F}$  are connected as shown in the figure, and charged by a 100 V battery. Find:

- The equivalent capacitance of the system.
- The total charge of the system.
- The potential difference,  $U_3$ .
- The charge  $q_1$ .



### Solution:

- a)  $C_1$  and  $C_2$  are connected in parallel and  $C_3$  is connected in series.

A system that consists of capacitors connected in series and in parallel, as in this example is called a complicated combination. In complicated combinations in order to find the equivalent capacitance we use the rules for series and parallel combinations.

Let us find the equivalent capacitance of the system.

Capacitors  $C_1$  and  $C_2$  are connected in parallel and have an equivalent capacitance  $C'$ .


$$C_{12} = C_1 + C_2 \quad C_{12} = 1 + 2 \quad C_{12} = 3\ \mu\text{F}$$

The new system is as shown in the figure.

The capacitors of capacitance  $C_{12}$  and  $C_3$  are connected in series and have an equivalent capacitance of  $C_{\text{eq}}$ , thus,

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_{12}} + \frac{1}{C_3} = \frac{1}{3} + \frac{1}{6} = \frac{1}{2}$$

$$C_{\text{eq}} = 2\ \mu\text{F}$$

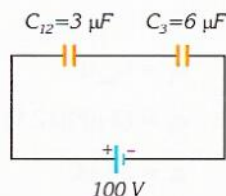

- b) The total charge of the system is

$$q_t = C_{\text{eq}} U = (2\ \mu\text{F})(100\ \text{V}) \quad q_t = 200\ \mu\text{C}$$

- c) Since charges on capacitors connected in series are equal, the charge on capacitor  $C_{12}$  and  $C_3$  is equal to the total charge of the system, which is  $q_t = 200\ \mu\text{C}$ .

Therefore, from

$$q_3 = C_3 U_3 \quad 200\ \mu\text{C} = 6\ \mu\text{F} U_3$$

$$\text{Thus, } U_3 = \frac{200\ \mu\text{C}}{6\ \mu\text{F}} = \frac{100}{3}\ \text{V}$$

- d) The charge  $q_1$  on  $C_1$  is,

$$q_1 = C_1 U_1$$

$$\text{and } U_1 = U_2 = 100 - \frac{100}{3} = \frac{200}{3}\ \text{V}$$

$$\text{Therefore, } q_1 = (1\ \mu\text{F}) \left( \frac{200}{3}\ \text{V} \right)$$

$$q_1 = \frac{200}{3}\ \mu\text{C}$$

## Question 7

Two capacitors  $C_1$  and  $C_2$  are connected to the terminals of a battery, as shown in the figure. Find the energy stored in capacitor  $C_1$ .

### Solution

$$W = \frac{1}{2} q_1 U_1 = \frac{1}{2} \frac{q_1^2}{C_1}$$

$$q_1 = q_2 = q_t$$

$$q_t = C_{\text{eq}} U$$

$$\frac{1}{C_{\text{eq}}} = \frac{1}{C_1} + \frac{1}{C_2} = \frac{1}{12\ \mu\text{F}} + \frac{1}{4\ \mu\text{F}}$$

$$C_{\text{eq}} = 3\ \mu\text{F}$$

$$q_t = (3\ \mu\text{F})(24\ \text{V}) = 72\ \mu\text{C}$$

$$q_1 = q_t = 72\ \mu\text{C}$$

$$W = \frac{1}{2} \frac{q_1^2}{C_1} = \frac{1}{2} \frac{(72 \times 10^{-6}\ \text{C})^2}{12 \times 10^{-6}\ \text{F}}$$

$$W = 2.16 \times 10^{-4}\ \text{J}$$

